

# RCA RADOTRON COMPANY, INC.

A RADIO CORPORATION OF AMERICA SUBSIDIARY

HARRISON

NEW JERSEY



OFFICE OF MANAGER

201 N. Front Street  
CAMDEN, N. J.

EQUIPMENT SALES  
ENGINEERING SERVICE DIVISION

APPLICATION NOTE No. 43

October 17, 1934

APPLICATION NOTE  
ON  
CATHODE-RAY CURVE-TRACING APPARATUS  
FOR  
ALIGNING TUNED CIRCUITS

"Visuals" or curve-tracing devices for showing the resonance curves of the intermediate- or radio-frequency stages of broadcast receivers have been in use for some time. Some manufacturers have installed enough "Visuals" to align their entire production. Others have installed one or more for aligning part of the production and for checking the work of aligners equipped with meter indicators.

The "Visual" is particularly useful where coupling is such that a double-peaked resonance curve is obtained, since the depth of the valley between the peaks is difficult to determine unless a plot of the curve can be examined. Such a plot is, of course, constantly before the "Visual" aligner so that the effect of coupling or tuning adjustments can be observed during the adjusting process. However, the cost of these curve-tracing devices has in many instances made their use impracticable and has made it necessary to resort to slower methods of checking the design and production of the intermediates. In contrast to high-priced apparatus employing the string galvanometer, cathode-ray apparatus is comparatively inexpensive and will give better results.

Some of the advantages of a cathode-ray "Visual" over the string-galvanometer type are:

1. The trace is more brilliant and does not require an awkward hood for observations in daylight.
2. Overload does not damage the apparatus but merely causes the beam to deflect off the screen.

Copyright, 1934, by  
RCA Radiotron Co., Inc.



APPLI CATION NOTES

3. The apparatus can be made portable.

4. The cost of the apparatus is low.

A resonance curve tracer employing the type 906 cathode-ray tube has been set up and operated in the laboratory of the RCA Radiotron Co. This device is designed to cover a range of intermediate frequencies of 100 kc to 500 kc and has an amplifier-detector section which is practically flat over the entire range. Since it is believed that a "Visual" of this type will be of distinct value to many laboratories as well as to manufacturers and service men who desire to improve their testing facilities, a detailed description of the instrument is given in this NOTE. Figure 1 is the schematic circuit diagram while Figure 2 shows the functional layout and a suggested arrangement for a portable resonance curve tracer. It should be borne in mind that the principles and methods involved in this application can be applied to obtain the curves of any form of tuned circuit and that the frequency range is not limited to the 100-500 kc of the apparatus illustrated.

A resonance curve is a plot of the voltage output of a tuned stage for a given frequency band. To obtain this curve, it is necessary to have a voltage source, which in this instance is the oscillator  $T_2$  of Figure 1, and to have a source of variable frequency covering a range which extends above and below the resonant frequency. The frequency variation to sweep across the frequency range of the tuned circuit can be accomplished manually by hand manipulation of a condenser or it can be speeded up to thirty times a second as is done in this case by means of an 1800 RPM motor. The fluctuating output voltage of the stage is then amplified, rectified, and again amplified, and finally applied to one set of the deflecting plates of a cathode-ray tube. The other set of deflecting plates is supplied with the sweep-frequency voltage.

The frequency sweep is produced by a motor of about 1/20 hp or more driving a rotating condenser  $C_2$  of maximum capacitance of 0.00035  $\mu$ f. A range switch  $S_2$  connects different values of capacitance  $C_3$ ,  $C_4$ ,  $C_5$ , etc., in series with  $C_2$  to adjust the sweep for different frequency ranges. The oscillator is tuned by adjusting  $C_1$ .

A contactor on the motor shaft controls the linear-sweep voltage by periodically short-circuiting condenser  $C_7$ . Condenser  $C_7$  charges linearly with time during the half revolution that condenser  $C_2$  sweeps the frequency. During the remaining half revolution, condenser  $C_7$  is short-circuited and  $C_2$  returns to the initial position.

The rheostat  $P_3$  in the cathode circuit of Tube  $T_1$  controls the rate of charge of condenser  $C_7$ . When  $P_3$  is properly adjusted, the contactor on the motor causes the voltage of condenser  $C_7$  to return to zero somewhat before the condenser becomes fully charged. When  $P_3$  is adjusted for too slow a charging rate, the sweep, as viewed on the screen of the cathode-ray tube, returns to zero before the full width of the screen has been traversed. On the other hand, if  $P_3$  is adjusted so that the charging rate is too high, the

sweep terminates with the condenser fully charged before the contactor has returned it to zero. Considerable distortion of the resonance curve traced on the screen results from this latter adjustment due to non-linearity at the end of the sweep.

The proper adjustment of  $P_3$  causes a full sweep across the screen without any bright spot occurring at the end of the sweep. The appearance of a bright spot is due to the beam remaining in one position for a greater length of time than in other positions. A bright spot should appear at the beginning of the sweep since the beam remains there for one-half of the cycle. At the end of the sweep, no spot should appear when  $P_3$  is properly adjusted.

The centering of the pattern on the screen is accomplished by adjusting the knob of potentiometer  $P_4$ .

The frequency-range switch  $S_2$  and the tuning condenser  $C_1$  should be adjusted so that the resonance characteristic appears in the center of the sweep on the screen. As condenser  $C_1$  is varied, the resonance characteristic is shifted along the sweep axis. The best value of  $C_1$  is that which centers the resonance curve on the sweep range.

The input to the grid of the i-f stage to be tested is connected to the contact terminal of potentiometer  $P_5$ . The test signal can be adjusted by means of  $P_5$  to give a suitable height of resonance curve. The range switch  $S_3$  reduces the signal when an overall test of two or more i-f stages is made.

When intermediates are to be aligned, the output voltage from the plate of the tube following the i-f stage is connected through a blocking condenser in series with a low resistance of approximately 1000 ohms to the amplifier circuit as shown in Figure 2. When the tube following the i-f stage is a diode detector, the resistance can be eliminated. In this case, the input lead is connected to the high-potential end of the diode load resistance. Sufficient i-f voltage is generally present across the by-pass condenser of the diode load resistor to give a deflection on the cathode-ray tube. Since the diode load is by-passed, there is no capacity effect from the connecting leads and the resonance adjustment does not change with their removal. The resonance curve obtained on the screen of the cathode-ray tube represents audio frequency and, hence, appears not as a modulation envelope but as a single-line curve above the zero axis.


The constants of the oscillator circuit will depend somewhat upon the arrangement of the wiring, distributed capacitance, etc. In order to realize the full operating range of frequencies from 100 kc to 500 kc, it is important to have tuning condensers with low minimum capacitances, and to keep wiring capacitances at a minimum. The exact values for the constants of the oscillator circuit are best determined by actual test after the apparatus is in operation. Suggested values for these constants are as follows:

$C_1 = 150$	$\mu\mu\text{f}$ maximum	
$C_2 = 350$	$\mu\mu\text{f}$	" (Ball-bearing type)
$C_3 = 0.00005$	$\mu\text{f}$	
$C_4 = 0.00005$	$\mu\text{f}$	
$C_5 = 0.0001$	$\mu\text{f}$	
$C_6 = 0.00035$	$\mu\text{f}$	
$L_1 = 2.0$	millihenries	
$L_2 = 2.0$	"	
$L_3 = 5.0$	"	

The inductances are closely coupled.



Desirable characteristics for the oscillator are uniform voltage output especially throughout the sweep range, and frequency change proportional to the angular rotation of the frequency-sweep condenser  $C_2$ . This condenser should preferably be one of the straight-line-frequency type, although an ordinary semi-circular plate condenser is easier to balance mechanically in order to avoid vibration. The latter, however, is satisfactory for the usual alignment purposes; that is, with it no distortion of the resonance curve is noticeable to the eye, although it could not be depended upon for precise measurements.

Care should be taken to select a variable condenser that is rugged in construction and revolves on ball bearings. Contact with the rotor can be made by means of a brush or other smooth-riding pressure contact on the condenser shaft. The short-circuiting contactor is a standard automotive ignition breaker. It is operated by a cam on the motor shaft. A bakelite drum having a metal insert in its periphery can be used as a shorting device, if it is desired.

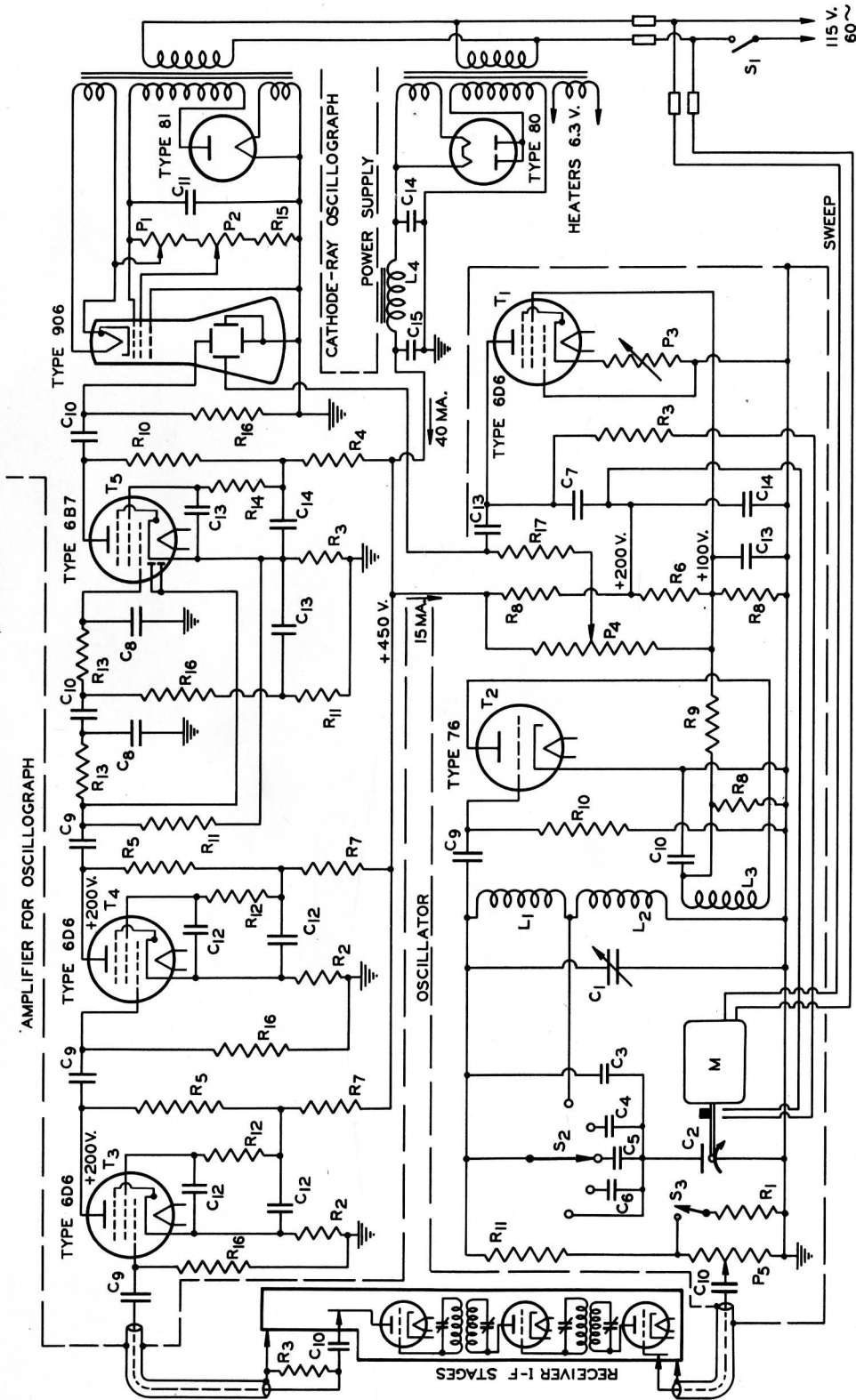

- C<sub>1</sub> = MAIN TUNING CONDENSER
- C<sub>2</sub> = FREQUENCY-SWEEP CONDENSER
- C<sub>3</sub> = FREQUENCY-RANGE CONDENSER
- C<sub>4</sub> = FREQUENCY-RANGE CONDENSERS
- C<sub>5</sub> = FREQUENCY-RANGE CONDENSERS
- C<sub>6</sub> = FREQUENCY-RANGE CONDENSERS
- C<sub>7</sub> = 0.5 μf
- C<sub>8</sub> = .0001 μf
- C<sub>9</sub> = .0002 μf
- C<sub>10</sub> = 0.1 μf
- C<sub>11</sub> = 1.0 μf
- C<sub>12</sub> = 2.0 μf
- C<sub>13</sub> = 4.0 μf
- C<sub>14</sub> = 8.0 μf
- C<sub>15</sub> = 16.0 μf
- R<sub>1</sub> = 50 OHMS
- R<sub>2</sub> = 300 OHMS
- R<sub>3</sub> = 1000 OHMS
- R<sub>4</sub> = 5000 OHMS
- R<sub>5</sub> = 10000 OHMS
- R<sub>6</sub> = 11000 OHMS
- R<sub>7</sub> = 14000 OHMS
- R<sub>8</sub> = 15000 OHMS
- R<sub>9</sub> = 25000 OHMS
- R<sub>10</sub> = 50000 OHMS
- R<sub>11</sub> = 100000 OHMS
- R<sub>12</sub> = 120000 OHMS
- R<sub>13</sub> = 200000 OHMS
- R<sub>14</sub> = 300000 OHMS
- R<sub>15</sub> = 500000 OHMS
- R<sub>16</sub> = 1 MEGOHM
- R<sub>17</sub> = 5 MEGOHMS
- L<sub>3</sub> = 40 HENRIES
- M = MOTOR, 1/20 H P - 1800 R.P.M
- S<sub>1</sub> = POWER-SUPPLY SWITCH
- S<sub>2</sub> = FREQUENCY-RANGE SWITCH
- S<sub>3</sub> = TEST-SIGNAL-RANGE SWITCH
- P<sub>1</sub> = 50 000 OHMS, BRILLIANCE-CONTROL POTENTIOMETER
- P<sub>2</sub> = 200 000 OHMS, FOCUSING-CONTROL POTENTIOMETER
- P<sub>3</sub> = 50 000 OHMS, TIME-SWEEP -CONTROL POTENTIOMETER
- P<sub>4</sub> = 200 000 OHMS, CENTERING-CONTROL POTENTIOMETER
- P<sub>5</sub> = 400 OHMS, TEST-SIGNAL-CONTROL POTENTIOMETER

FIG. 1

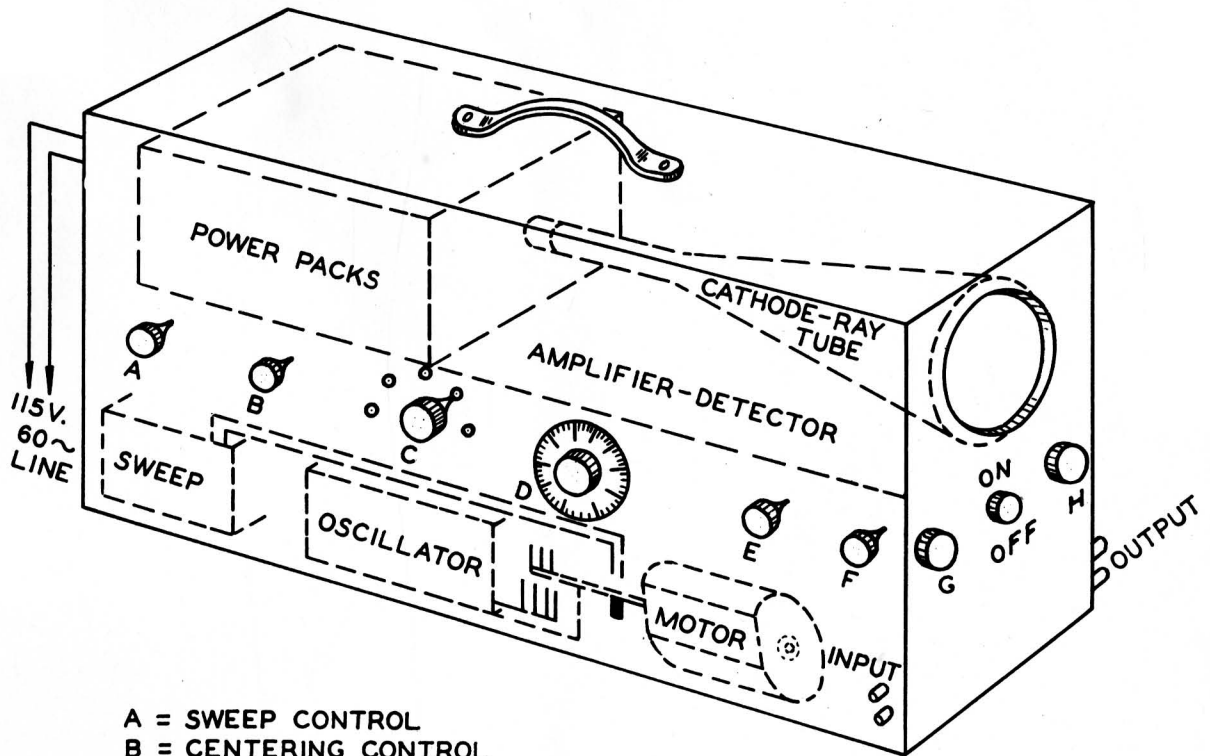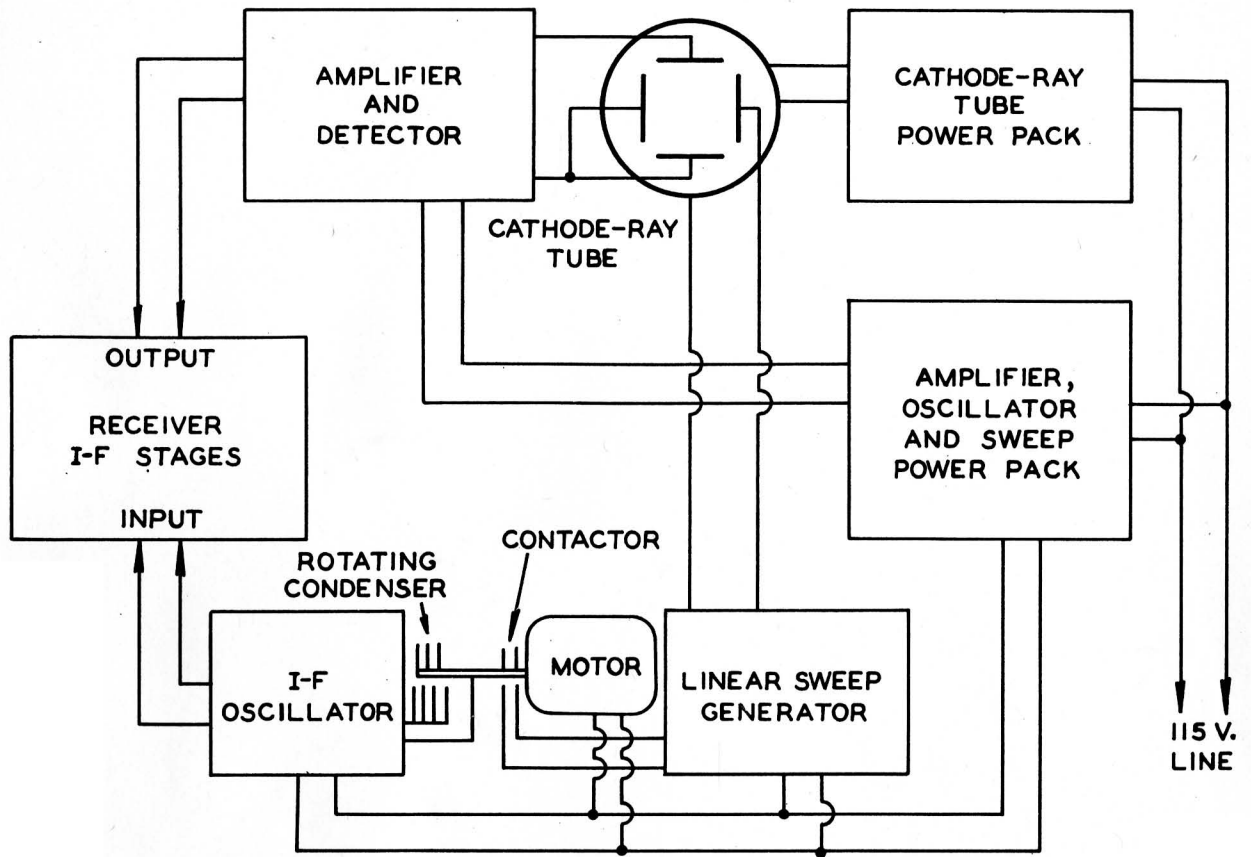

- |                             |                        |
|-----------------------------|------------------------|
| A = SWEEP CONTROL           | F = SIGNAL CONTROL     |
| B = CENTERING CONTROL       | G = FOCUS CONTROL      |
| C = FREQUENCY-RANGE CONTROL | H = BRILLIANCE CONTROL |
| D = FREQUENCY CONTROL       |                        |
| E = RANGE CONTROL           |                        |

FIG. 2