

AN - 149
March 1, 1951

Application of Transformer RCA-225T1 in Deflection System for Wide-Angle Large-Screen Kinescopes

A deflection system using the new ferrite-core transformer, RCA-225T1, has been developed to supply adequate horizontal deflection and an anode voltage of 16 kilovolts for kinescopes such as the RCA-17CP4 and RCA-20CP4 having horizontal-deflection angles of about 66 degrees. The tubes required for the horizontal-deflection-and-high-voltage circuit are one 6BQ6-GT or 6AU5-GT beam power amplifier, one 6WL4-GT damper diode, and one 1B3-GT high-voltage rectifier. Transformer RCA-225T1 is so designed that the power for the vertical-deflection circuit may be obtained from the boosted B-voltage supply. The power input required for the horizontal-deflection-and-high-voltage and vertical-deflection circuits totals approximately 29 watts from a 280-volt B-supply when a 6BQ6-GT is used, or 31 watts from a 300-volt B-supply when a 6AU5-GT is used.

General circuit design considerations for the use of the RCA-225T1 are the same as those for the RCA-224T1 and are described at some length in RCA Application Note AN 148. The deflecting yoke, RCA-209D1; the linearity control, RCA-209R1; and the vertical-deflection circuits for the RCA-225T1 are the same as those used with the RCA-224T1. The recommended horizontal-deflection circuit for the 225T1 shown in Fig.1 is essentially the same as the circuit for the 224T1. Special considerations in the use of the 225T1 are discussed below.

Width Control

An inductive width control may be used, connected to terminals 1 and 3 of the 225T1. When this control has the recommended inductance range (1.5 to 13 millihenries), the maximum width reduction is approximately 12 per cent and the corresponding high-voltage reduction is approximately 400 volts.

The deflection circuit is well suited to methods of width control in which power input to the circuit is varied. One such method is to insert an unbypassed variable resistor in series with the B-supply lead



to the deflection circuits. Another is to add a variable resistor in series with the screen-grid resistor, R_{15} . A disadvantage of these methods is that the high-voltage is reduced; an advantage is that appreciably less current is required by the deflection circuits. For example, with any of the power-control methods the no-load kinescope anode voltage at normal width setting is approximately 14.5 kilovolts and the cathode current of the horizontal-output tube is approximately 80 milliamperes (the corresponding figures with an inductive width control are 16 kilovolts and 95 milliamperes). By adjustment of the power control, variations in line voltage and components can be compensated for, so that for normal picture width the no-load high voltage and the cathode current of the horizontal-output tube are maintained substantially constant at the above figures.


Lead Dress

The step-up ratio of the 225T1 transformer is such that a kinescope anode voltage of 16 kilovolts may be obtained. Because of this step-up ratio any capacitance between the 1B3-GT plate and the chassis has a 30 times greater effective value at the yoke. If this effective capacitance is excessive, horizontal-retrace time is increased and the high voltage is decreased. Consequently, it is important to keep the 1B3-GT plate lead short and to mount the 1B3-GT in such a manner that stray capacitance from plate to chassis is minimized.

Drive Requirements

To obtain adequate deflection and high-voltage output from any horizontal-deflection circuit without excessive power input and excessive dissipation in the horizontal-output tube, a sawtooth voltage of proper amplitude and waveform must be applied to the grid of the horizontal-output tube. The proper amplitude is that which results in near class B operation. Insufficient sawtooth voltage yields more nearly class A operation, and therefore results in reduced efficiency and a consequent reduction in the deflection voltage and high-voltage output. Excessive sawtooth voltage produces class C operation, which causes a localized cramping and a resultant white line near the center of the raster. The desired sawtooth amplitude may be determined by adjusting the drive control to increase the amplitude until a white line appears near the center of the raster and then reducing the drive until the white line just disappears.

The waveform of the driving sawtooth voltage is determined in the design of the horizontal-oscillator circuit and no service adjustment is needed. The criterion for proper sawtooth waveform is circuit efficiency. If the designer uses a horizontal-oscillator circuit other than that shown in Fig.1, he should try various component values in the horizontal-oscillator circuit until the combination is found which produces the most high-voltage output with the least cathode current in the horizontal-output tube. The data in Table I indicate the efficiency which can be obtained. The shape of the sawtooth voltage waveform on an oscilloscope is not a satisfactory criterion for waveform adjustment. Significant changes in circuit efficiency can be obtained with such subtle changes in sawtooth waveform that the effects on the oscilloscope waveform are not readily perceptible.

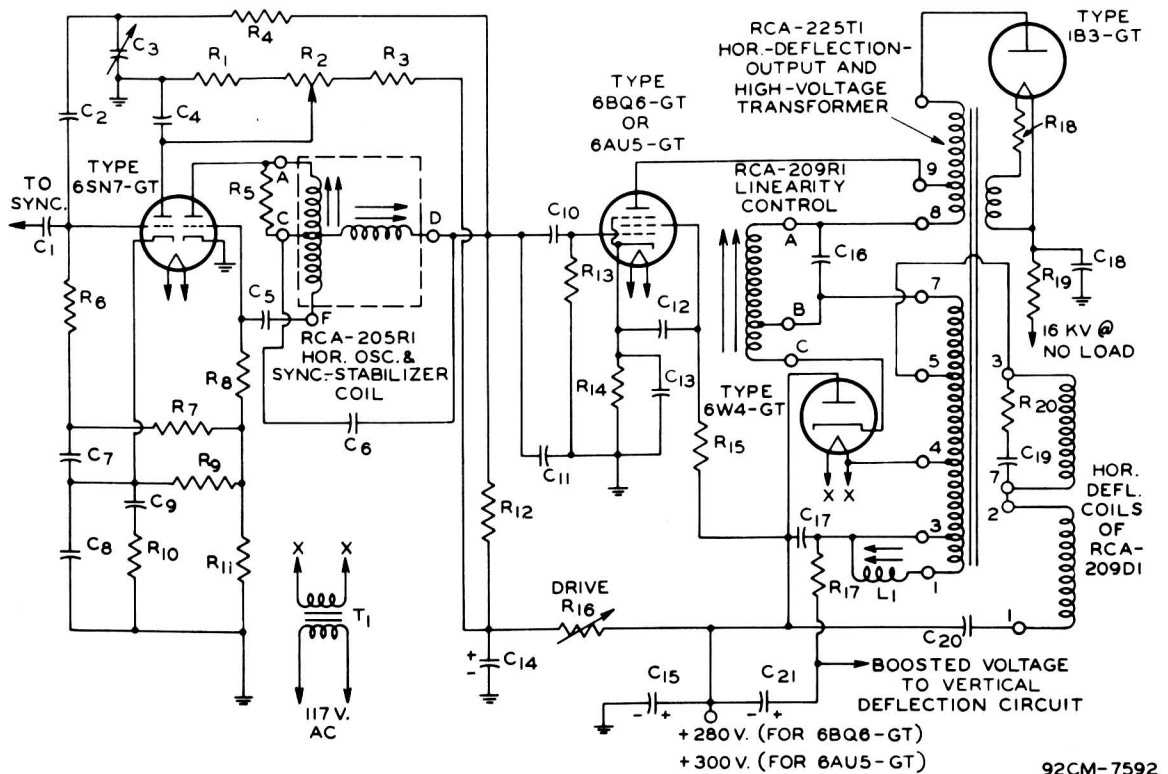

- C1 C2: 82 μf , 500 v., mica
- C3: Locking range control, 8-70 μf , mica trimmer
- C4: 0.05 μf , 400 v.
- C5: 330 μf , 500 v., mica
- C6: 0.01 μf , 600 v., oil-filled
- C7: 0.05 μf , 400 v.
- C8: 0.02 μf , 400 v.
- C9: 0.5 μf , 400 v.
- C10: 0.003 μf , 600 v.
- C11: 820 μf , 500 v., mica
- C12: 0.1 μf , 400 v.
- C13: 0.5 μf , 200 v.
- C14: 10 μf , 300 v., electrolytic
- C15: 20 μf , 300 v., electrolytic

- C16: 0.04 μf , 400 v.
- C17: 0.03 μf , 600 v.
- C18: 500 μf , 20 kv.
- C19: 56 μf \pm 5%, 800 v.
- C20: 0.1 μf , 400 v.
- C21: 10 μf , 250 v., type DEE or equivalent
- R1: 0.12 megohm, 1 watt
- R2: Hold Control, 50000-ohm potentiometer, 2 watts
- R3: 47000 ohms, 1 watt
- R4 R8: 0.15 megohm, 1 watt
- R5: 8200 ohms, 0.5 watt
- R6: 0.33 megohm, 0.5 watt
- R7: 0.82 megohm, 0.5 watt
- R9: 82000 ohms, 1 watt
- R10: 3900 ohms, 0.5 watt
- R11: 0.33 megohm, 1 watt

- R12: 68000 ohms, 1 watt
- R13: 0.47 megohm, 0.5 watt
- R14: 150 ohms, 2 watts
- R15: 8200 ohms approx., 2 watts
- R16: Drive control, 25000-ohm potentiometer, 2 watts
- R17: 1000 ohms, 1 watt
- R18: 3.9 ohms, 0.5 watt
- R19: 50000 ohms min., 1 watt
- R20: 10000 ohms, 0.5 watt
- T1: Heater transformer insulated for 1.5 kv peak
- L1: Width control, min. inductance, 1.5 mh, ferrite core

92CM-7592

NOTE: Terminals A, B, and C of the RCA-209R1 Linearity Control can be identified by resistance measurements. The resistance between terminals A and B is approximately 4 ohms and the resistance between terminals B and C is approximately 1.5 ohms.

Fig. 1 - Horizontal-Deflection and High-Voltage Circuit.

Vertical Deflection

The vertical-deflection circuits may be operated from the boosted B-supply, provided the current drain is not more than 12 milliamperes. Any larger current drain reduces the scanning amplitude and the high-voltage output. The relatively high boosted voltage permits the design of a vertical-deflection circuit of good efficiency. When a 6S4 vertical-output tube, a 209D1 yoke, and a vertical-output transformer having an 18:1 turns ratio are used, adequate vertical deflection is obtained with a 6S4 plate current of approximately 11 milliamperes.



Typical Operation

Table I shows typical operating conditions for the circuit of Fig.1 with an average 6BQ6-GT, a line voltage of 117 volts, and with maximum width adjustment. For purposes of evaluating circuit performance, the following values should be measured: the B-voltage, the 6BQ6-GT cathode current, the 6BQ6-GT screen current, the 6BQ6-GT screen voltage, the current drawn from the boosted-voltage supply, and the voltage of the high-voltage supply.

Table I - Typical Operation of Circuit in Fig.1*

B-Voltage.	280	volts
High Voltage:		
At Zero Beam Current	16	kilovolts
At 140 μ a Beam Current	14.8	kilovolts
Boosted Voltage [●]	520	volts
Current from Boosted Voltage Supply.	11	milliamperes
Retrace Time	8.3	microseconds
6BQ6-GT		
Cathode Current.	93.7	milliamperes
Plate Current.	80.0	milliamperes
Grid-No.2 Current.	13.7	milliamperes
Grid-No.2 Voltage.	146	volts
Grid-No.2 Input.	2.0	watts
Grid-No.1 Voltage [▲]	-32	volts
Peak Plate Voltage	4350	volts
6W4-GT		
Plate Current.	91	milliamperes
Peak Inverse Plate Voltage	2400	volts
Peak Heater-to-Cathode Voltage	1600	volts
1B3-GT		
Peak Inverse Plate Voltage	18.7	kilovolts

* At a line voltage of 117 volts with maximum width adjustment. All values are at zero kinescope beam current unless otherwise noted.

● Measured at terminal 3 of RCA-225T1.

▲ Composed of 14 volts cathode bias and 18 volts grid-resistor bias.

When a 6AU5-GT is used, the no-load value of the high voltage is 16 kilovolts for the following 6AU5-GT operating conditions: B-voltage, 300 volts; screen voltage, 195 volts; screen current, 10.5 milliamperes; and cathode current, 91 milliamperes.



ERRATUM NOTICE

for

Application Note AN-149 'Application of Transformer RCA-225T1 in Deflection System for Wide-Angle Large-Screen Kinescopes.'

Page 3, Fig.1 - Horizontal-Deflection and High-Voltage Circuit. The value shown in the parts list for resistor R20 is incorrectly given as 10000 ohms, 0.5 watt; the correct value of R20 is 1000 ohms, 0.5 watt.