



## Measurement of Dissipation in Plate of Horizontal-Deflection Output Tube

In the design of television horizontal-deflection circuits, a knowledge of the power dissipated in the plate of the horizontal-output tube enables the designer to make sure that the tube rating is not exceeded and that circuit efficiency is high. This Note\* describes a method of determining this dissipation. In its simplest form, the method involves the measurement of only four factors: (1) the rms current in the horizontal-deflecting windings; (2) the total dc resistance of these windings; (3) the rms diode current; and (4) the average plate current of the horizontal output tube. Although this method was developed for the popular circuit of Fig.1, in its most general form (equation 1) it is applicable to all deflection circuits. When separate-winding output transformers are used, however, the transformer copper losses and the plate dissipation due to leakage inductance should be determined.

### Components of Plate Dissipation

The effective load in the plate circuit of the horizontal-output tube in Fig.1 consists of a reactive and a resistive load. The reactive load represents the power terms  $P_S$ ,  $P_X$ , and  $P_R$ , where  $P_S$  is the power lost due to leakage inductance in the transformer,  $P_X$  is the power output from the boost voltage, and  $P_R$  is the power absorbed by the deflection system during retrace (this power is partly dissipated in the windings and partly converted to high-voltage power output). The resistive load consists of  $R_p$  which represents both the diode plate loss and the copper losses of the circuit during scanning.

The plate dissipation of the power tube supplying these loads has three components. One is a fraction of  $P_S$ , another is a fraction of the power input to  $R_p$ , and the third is the so-called "minimum" plate power

\* This note is based on material contained in an article entitled "Characteristics of High-Efficiency Deflection and High-Voltage Supply Systems for Kinescopes" by O.H. Schade. This article appeared in the March 1950 issue of the RCA REVIEW.



loss determined from the plate characteristic. Methods for determining these components are developed below.

### Leakage-Inductance Component

The amount of plate dissipation due to leakage inductance is difficult to measure. When the transformer is of the autotransformer type, this dissipation can be assumed to be approximately 0.5 watt in most cases. If desired, however, it may be determined more accurately from an expression discussed later in the Note. The more accurate determination may be advisable when the approximate calculation indicates that the plate dissipation is close to the tube rating.

### Resistive Component

For all practical circuits and plate-current waveforms (Fig. 2), the conversion efficiency is approximately 0.65, or 1/1.55. In other words,  $P_R$ , the dc power input to  $R_p$ , equals 1.55  $P_{R_p}$ , where  $P_{R_p}$  is the power output dissipated in  $R_p$ . The plate dissipation due to  $R_p$  is  $P_R$  minus  $P_{R_p}$ , or 0.55  $P_{R_p}$ . Power  $P_{R_p}$  is the sum of the diode plate dissipation and all copper losses in the system. The copper losses,  $P_{Cu}$ , in the transformer and horizontal-deflecting windings are readily determined from the  $I^2R$  formula after the rms currents in the various windings and the corresponding dc resistance of the windings have been measured. To reduce the number of measurements, it may be assumed that  $P_{Cu} = 1.5 P_{Cu_h}$ , where  $P_{Cu_h}$  is the copper loss in the horizontal-deflecting windings of the yoke. This approximation is valid when an autotransformer is used.

The diode plate loss,  $P_{p2}$ , can be computed from the equation:

$$P_{p2} = 0.18 i_{p2} e_{p2}$$

After  $I_{b2}$ , the rms current of the diode, is measured with a thermal-type meter, the peak diode current,  $i_{p2}$ , can be determined from the equation:

$$I_{b2} = 0.41 i_{p2}$$

Alternatively,  $i_{p2}$  can be measured directly by means of a calibrated oscilloscope and resistor. The peak plate voltage,  $e_{p2}$ , is then found on the static characteristic of the diode at the point corresponding to a plate current of  $i_{p2}$ .

The values of  $P_{lin}$ , the copper loss in the linearity transformer, is approximately 25 per cent of the power it handles, i. e.,

$$P_{lin} = 0.25(P_{p2} + P_{Cu}/2)$$

This relationship holds for linearity controls with either single or multiple windings.

### "Minimum" Component

The "minimum" portion of the plate power loss is the product of  $I_{b1}$ , the average plate current, and  $E_{min}$ , the minimum value that the plate voltage attains cyclically. The value of  $E_{min}$  should be adjusted to come slightly above the knee of the plate characteristic, as discussed

later. Next,  $I_{b1}$  is measured with a dc meter. Because the peak current handled by the tube is closely equal to three times  $I_{b1}$ , the peak current  $i_{p1}$  is determinable. The value of  $E_{min}$  can then be found from the plate characteristic; it is the voltage that causes a plate current of  $i_{p1}$  when the control-grid voltage reaches its most positive swing (usually zero volts).

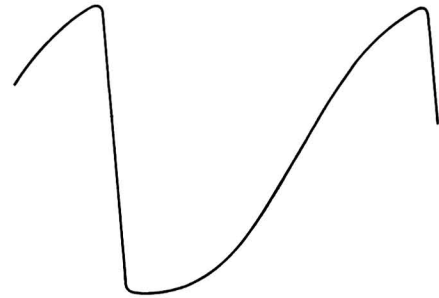
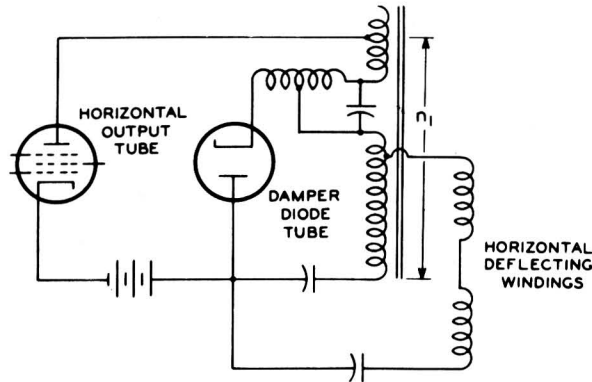


Fig. 1 - Partial Schematic of Typical Horizontal-Output Circuit

Fig. 2 - Typical Waveform of Current in Horizontal-Output Tube

### Total Plate Dissipation

The total plate dissipation of the horizontal-output tube is now seen to be the following:

$$\begin{aligned} \text{Plate dissipation} &= E_{min}I_{b1} + 0.55 [P_{Cu} + P_{p2} + 0.25 (P_{Cu}/2 + P_{p2})] + 0.5 \\ &= E_{min}I_{b1} + 0.62P_{Cu} + 0.69P_{p2} + 0.5 \end{aligned} \quad (1)$$

or, more approximately, on the previously discussed assumption that  $P_{Cu} = 1.5P_{Cu_h}$ ,

$$\text{Plate dissipation} = E_{min}I_{b1} + 0.93P_{Cu_h} + 0.69P_{p2} + 0.5 \quad (2)$$

### Precise Evaluation of Leakage Component

The value of  $P_{sp}$ , the plate dissipation due to leakage inductance, which is assumed above to be 0.5 watt, may be computed, if desired, from the following expression.

$$P_{sp} = (E_{bb} - E_{min} - E_{Rp}) \left(1 - \frac{L}{L + L_s}\right) (I_{b1}) - 0.5fL_s(i_{p1})^2$$

where  $E_{bb}$  is the boosted voltage;  $L_s$  is the leakage inductance of the section of the transformer across which the horizontal-output tube is connected;  $L$  is the inductance of this section when the deflecting windings are connected in conventional fashion;  $f$  is the horizontal-scanning frequency, 15,750 cycles per second; and  $E_{Rp}$  is the voltage which causes the dc power input  $P_R$  to the load  $R_p$ , as determined from the equation:

$$E_{Rp} = 1.55P_{Rp}/I_{b1}$$



The magnitude of  $L$  is determined by measuring the inductance of transformer winding  $n_1$  (Fig. 1) with the deflection winding connected as shown. The value  $L_s$  is the inductance measured across  $n_1$  when the deflection windings are shorted out. In both cases the linearity transformer should be shorted out.

### Correct Operating Conditions

An excess value of  $B$  voltage,  $E_b$ , causes increased circuit losses (Fig. 3a); insufficient  $B$  voltage reduces the output. The correct  $E_b$  is that which causes  $E_{min}$  to fall slightly above the knee of the characteristic curve (Fig. 3b). A way to determine this correct operating condition follows. Apply a moderately excessive value of  $B$  voltage. Slowly reduce this voltage while holding all grid voltages constant. While the output power of the horizontal-output tube decreases slowly, the minimum tube drop is still above the knee of the curve. When, at length, any further decrease in  $B$  voltage causes a sudden sharp decrease in output and an increase in screen current,  $E_{min}$  has just passed below the knee of the curve. The value  $E_b$  at which this phenomenon occurs should be noted. The  $B$  voltage used in the design should be a few volts greater than this value, so that  $E_{min}$  will fall at or just above the knee.

### Sample Calculation

An example follows of the determination of plate dissipation. The circuit measured uses a 6BQ6-GT horizontal-output tube, a 6W4-GT damper diode, and an experimental autotransformer and yoke. The calculated dissipation is close to that obtained by a more time-consuming thermocouple method in which the dynamic plate loss is equated to the static plate loss that causes the bulb temperature to be the same as under dynamic conditions.

After  $E_{min}$  has been adjusted to come above the knee of the characteristic curve, the dc plate current  $I_{b1}$  is measured to be 83.5 milliamperes. From the relationship that  $i_{p1}$  equals  $3I_{b1}$  the calculated peak plate current is 250 milliamperes. From the characteristic curve,  $E_{min}$  corresponding to 250 milliamperes is 60 volts. The copper loss ( $P_{cu_h}$ ) in the horizontal-deflecting windings is determined from measurement of the rms current in the windings, 305 milliamperes, and of the resistance of the windings, 22 ohms. Therefore,

$$P_{cu_h} = I^2 R = (0.305)^2 \times 22 = 2.04 \text{ watts}$$


Dividing 0.41 into the rms diode current  $I_{b2}$ , measured at 164 milliamperes, gives the peak diode current  $i_{p2}$ , 400 milliamperes. From the 6W4-GT characteristic curve, the plate voltage for a current of 400 milliamperes is 29 volts. Therefore,

$$P_{p2} = 0.18 i_{p2} e_{p2} = 0.18 \times 0.4 \times 29 = 2.09 \text{ watts}$$


From equation 2,

$$\begin{aligned} \text{Plate dissipation} &= E_{min} I_{b1} + 0.93 P_{cu_h} + 0.69 P_{p2} + 0.5 \\ &= (60 \times 0.0835) + (0.93 \times 2.04) + (0.69 \times 2.09) + 0.5 \\ &= 8.85 \text{ watts} \end{aligned}$$

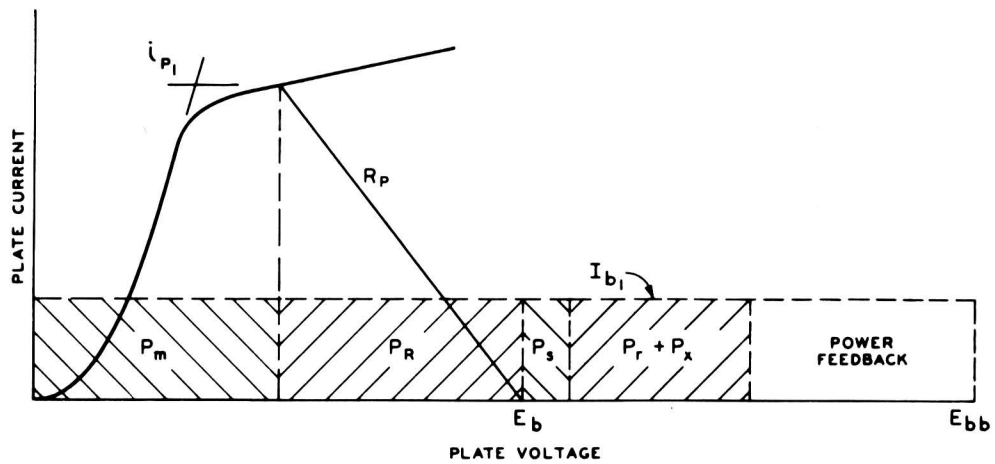The comparable value arrived at with the thermocouple method is 9.1 watts.



- a -

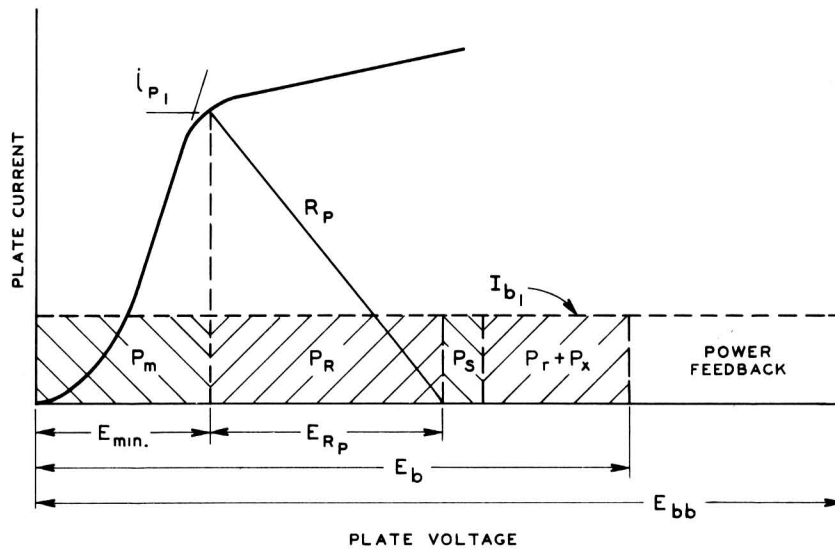

- b -

Fig. 3 - Plate Load Diagrams for Horizontal-Output Tube Under (a) Excessive B-supply Voltage, and (b) Correct B-supply Voltage. In these Diagrams,  $E_b$  is the B-supply Voltage and  $E_{bb}$  is the Boosted Voltage; the other Symbols are Defined in the Text

Devices and arrangements shown or described herein may use patents of RCA or others. Information contained herein is furnished without responsibility by RCA for its use and without prejudice to RCA's patent rights.