



15 So. FIFTH St., HARRISON, N. J.

NAME OF STREET

DESCRIPTION

THE STATE OF

# UNIFIED SALES--ENGINEERING SERVICE TO EQUIPMENT MANUFACTURERS

MEADE BRUNET, Manager HARRISON, NEW JERSEY

APPLICATION NOTE No. 33

January 31, 1934

#### APPLICATION NOTE

ON

THE RCA-800 IN CLASS B AUDIO AMPLIFIERS

The RCA-800 is a triode designed for use as a radio-frequency power amplifier or oscillator. It can also be used to advantage as a Class B audio-frequency amplifier where large power output is required. When two of these tubes are used in this way, 100 watts of audio power can be obtained.

In this application note, data are given for Class B operation of the RCA-800 with plate potentials of 750, 1000, and 1250 volts. The optimum plate-to-plate loads and transformer ratios for each condition of operating voltage are also shown. A pair of 2A3 or 45 tubes will supply maximum driver signal.

Typical operating conditions for two 800's in a Class B output stage are as shown:

#### TABLE I

Driver Tubes, Two 2A3's; Plate Volts, 250; Grid Volts, -45

	Bias	Driver Trans- former Ratio* Pri. to ½ Sec.		Plate Input Power(2 Tubes) Watts	Total Power Output Watts	Total Distor- tion Per Cent
750	-50	1.75 : 1.0	6400	160	90	7.3
1000	-55	2.0 : 1.0	12500	160	100	7.0
1250	-70	2.0 : 1.0	21000	160	106	7.0

#### TABLE II

Driver Tubes, Two 45's; Plate Volts, 275; Grid Volts, -56.

1000 -55 2.16: 1.0 12500 160 100 7.9

\*For approximately 80% peak-power efficiency.

Copyright, 1933 by RCA Radiotron Co., Inc.

Figures 1, 2, 3, and 4 show power output, per cent harmonics, d-c plate current, and d-c grid current versus RMS voltage on the grids of the drivers for each of the above tabulated operating conditions. Figure 5 shows the fidelity curve for the 1000-volt condition of Table I.

Figure 6 is the plate family for the 800.

Figure 7 is a circuit diagram of a typical Class B audio amplifier. Grid bias should be supplied from a source having good voltage regulation. A small-capacity storage battery is excellent for supplying this bias, since the action of this type of amplifier is usually such as to keep the battery charged. In general, a dry battery should not be used since it may polarize when grid current is drawn or it may have too high an internal resistance. If it is desired to use a rectifier arrangement, a rectifier with good voltage regulation should be used.

Transformer design specifications are given for three transformers, as follows:

- (1) #S-119 Input transformer for operation of two 800 tubes in a Class B system driven by two 2A3 tubes.
- (2) #S-121 Input transformer for operation of two 800 tubes in a Class B system driven by two 45 tubes.
- (3) #S-120 Output transformer for use with two 800's operated in a Class B system.

#S-120 is a modulation transformer designed to carry direct current. The secondary windings of this transformer provide a plate-to-plate load on the 800's of 12500 ohms when they are series-connected and shunted by 20000 ohms, or when they are parallel-connected and shunted by 5000 ohms. For loud-speaker operation, a transformer should be designed in accordance with the plate-to-plate loads given in the tabulation. This transformer should have the same primary inductance and the same space distribution of windings as the #S-120 but should not have an air gap.

The high voltage required for the operation of 800's is dangerous to the user and should be carefully insulated to protect him. The tubes should be operated in well-ventilated compartments provided with interlocks which automatically shut off the power during adjustment of the apparatus.

#### INPUT TRANSFORMER S-119\*

(For two 2A3 tubes operating in a push-pull system at plate volts = 250, grid volts = -45, and driving two 800 tubes, Class B.)

Core: Material - Super Dynamo Gauge #26 Allegheny Steel Co. or

equivalent

Punching - EI - 11

Window -  $.432" \times 1-5/16"$ 

Tongue - 7/8"
Stack - 1-5/16"
Joint - Lap

Net Section - 6.5 sq. cm.

Mean Length Magnetic Circuit - 15.6 cm.

Weight -1.5 lb.

Winding: Traverse and margin -1/8" + 1" + 1/8"

Max. depth - Primaries 40% - Secondary 60% of net winding

space

Primary #1: Turns - 870 - #35 enamelled

Location - over core Turns per layer - 145

Layers - 6

Insulation between layers - .0015" paper Insulation under winding - .063" paper

Primary #2: Turns - 870 - #35 enamelled

Location - over insulated secondary

Turns per layer-145 Layers - 6

Insulation between layers - .0015" paper Insulation over winding - .045" paper Insulation under winding - .025" paper

Mean length of turn of total Primary #1 and #2 - 6"

Resistance at 25°C of total Primary #1 and #2 - 300 ohms

Secondary: Turns - 1770 tapped at 885 turns - #33 enamelled

Location - over #1 Primary Turns per layer - 118

Layers - 15

Insulation between layers - .0015" paper Insulation under winding - .025" paper

Mean length of turn - 6"

Resistance at 25° C. - 204 ohms total

Efficiency at full load = 78.2%

Inductance of total primary = approx. 30 henries at full signal; higher at lower signal levels.

<sup>\*</sup>Our design identification number.

#### INPUT TRANSFORMER S-121\*

(For two 45 tubes operating in push-pull at plate volts = 275, grid volts = -56, and driving two 800 tubes, Class B.)

Core:

Material - Super Dynamo Gauge #26 Allegheny Steel Co. or

equivalent

Punching - EI - 11

Window - .432"  $\times 1-5/16$ "

Tongue - 7/8"
Stack - 1-5/16"
Joint - Lap

Net section - 6.5 sq. cm.

Mean length of magnetic circuit - 15.6 cm.

Weight - 1.5 lb.

Winding:

Traverse and margin - 1/8" + 1" + 1/8"

Primary #1:

Turns - 870 #35 enamelled

Location - over core Turns per layer - 145

Layers - 6

Insulation between layers - .0015" paper Insulation under winding - .063" paper

Primary #2:

Turns - 870 #35 enamelled

Location - over insulated secondary

Turns per layer - 145

Layers - 6

Insulation between layers - .0015" paper Insulation over winding - .012" paper Insulation under winding - .025" paper

Mean length of turn of Primary #1 and #2 in series - 6 \*Resistance at 25 °C of Primary #1 and #2 - 300 ohms

Secondary:

Turns - 2080 tapped at 1040 #34 enamelled

Location - over #1 Primary Turns per layer - 130

Layers - 16

Insulation between layers - .0015" paper Insulation under winding - .025" paper

Mean length of turn - 6"
Resistance at 25° C - 298 ohms

Efficiency at full load = 80%

Inductance of total primary = approximately 30 henries at full signal; higher at lower signal levels.

<sup>\*</sup>Our design identification number.

### OUTPUT TRANSFORMER S-120\* - For two 800's Class B

Core: Material - Super Dynamo #26 Allegheny Steel Co. or equivalent

Punching - LE - 5

Window - .925" x 3.0"

Tongue - 1.450" Stack - 2.9"

Joint - 0.015" spacing per leg. (See note A)

Net section - 25.4 sq. cm.

Mean length magnetic circuit - 29.2 cm.

Weight - 11.4 lbs.

Winding: Traverse and Margin - 1/8" + 2-11/16" + 1/8"

Max. depth of windings - use approx. 55% of net winding

space for total primary tapped at 1900T

Primary: Turns - 3800 #28 enamelled

Location - next to core

Turns per layer - 180

Insulation between layers - .003" paper
Insulation under winding - .063" cardboard

Mean length of turn - 10.9"

Resistance at 25° C - 234 ohms total

Secondary #1: Turns - 2450 #31 enamelled

Location - over primary

Turns per layers - 250 Layers - 10

Insulation between layers - .003" paper

Insulation under winding - .045" built up with empire cloth

Mean length of turn - 13.34"
Resistance at 25°C - 370 ohms

Secondary #2: Turns - 2450 #31 enamelled

Location - over #1 Secondary

Turns per layer - 250 Layers - 10

Insulation between layers - .003" paper

Insulation over winding - .020" built up with empire cloth

Insulation under winding - .030" " " " "

Mean length of turn - 14.62"
Resistance at 25°C. - 408 ohms

Efficiency - 89.1% with 20000 ohm load and 89.5% with 5000

ohm load at 60 cycles.

Inductance - Approximately 11.8 henries 1/2 primary with 100 ma. d.c. in total secondary (series connected) and 10% full signal volts at 100 cycles.

Note A - Center leg of LE-5 lamination should have gap as shown in Figure 8A or 8B.

<sup>\*</sup>Our design identification number.


OUTPUT TRANSFORMER S-120\* (continued)

Note B: Plate-to-plate load is 12500 ohms with a 20000-ohm load on the secondary when the secondaries are connected in series, or 5000-ohm load on the secondary when the parallel connection is used. Since the transformer is designed to modulate transmitting tubes imposing one of the two stated loads on the transformer, it is provided with an air gap to carry 100 ma. d.c. for the two secondaries connected in series, or 200 ma. for the parallel connection of the secondaries. In case of a secondary load without direct current, the air gap becomes unnecessary so that a smaller size of transformer can be employed to give the same efficiency.


<sup>\*</sup>Our design identification number.


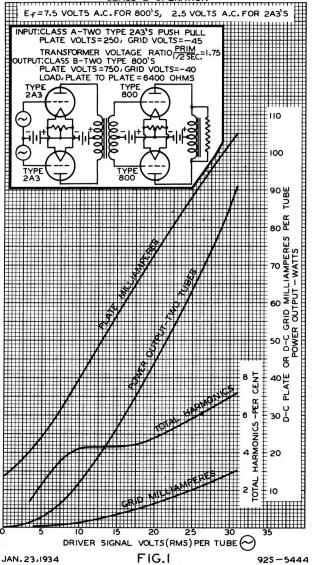
## OPERATION CHARACTERISTICS CLASS B OPERATION






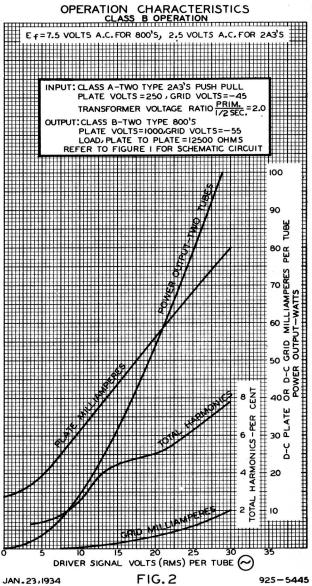



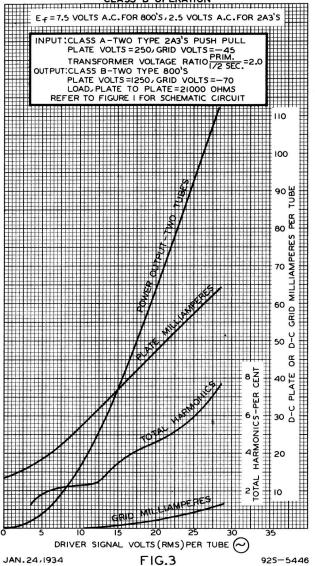
## OPERATION CHARACTERISTICS CLASS B OPERATION






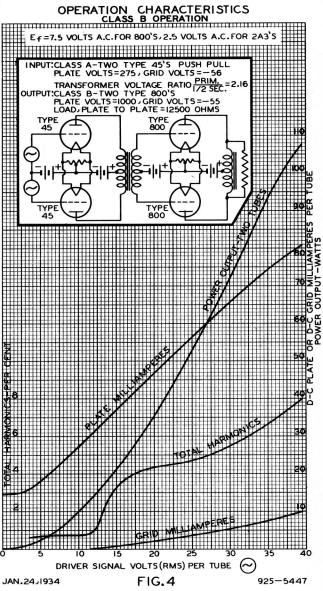

RCA RADIOTRON COMPANY, INC.

RCA RADIOTRON COMPANY, INC.



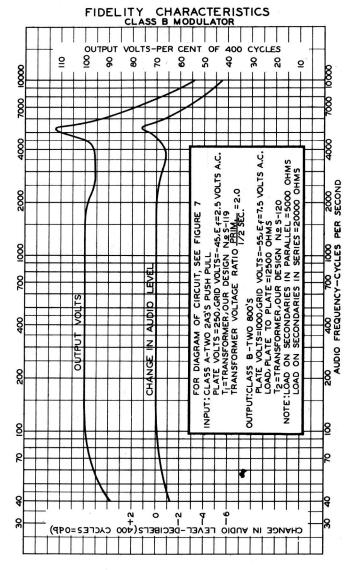


JAN. 24,1934

FIG.5

925-5448




### AVERAGE PLATE CHARACTERISTICS

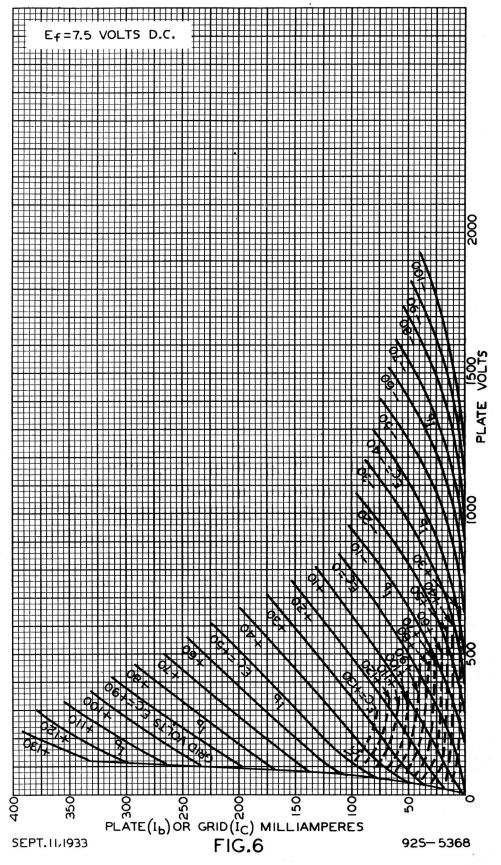


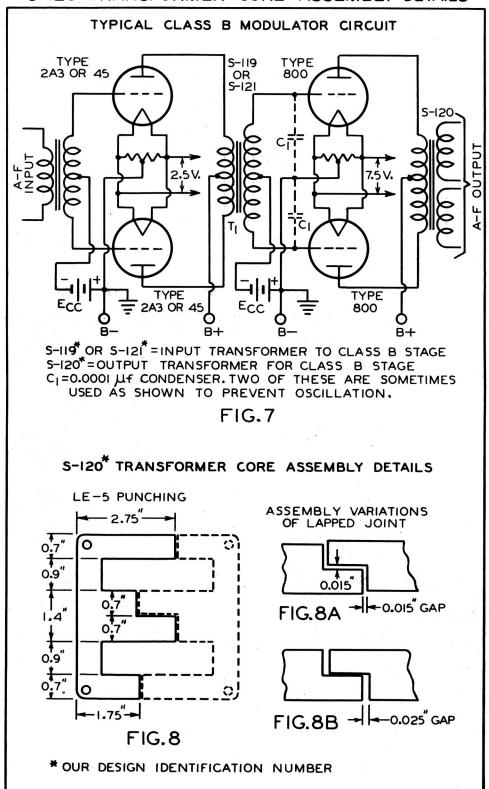
#### TYPICAL CIRCUIT FOR CLASS B MODULATOR S-120 TRANSFORMER CORE ASSEMBLY DETAILS



The license extended to the purchaser of tubes appears in the License Notice accompanying them. Information contained herein is furnished without assuming any obligations.