


VACUUM PRODUCTS INC.

Thermocouple Specialists

NOW!

20 YEARS EXPERIENCE

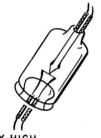A RELIABLE SOURCE FOR VACUUM THERMOCOUPLES!



INSULATED HEATER TYPE D.C. TO 50 M C.

ULTRA HIGH FREQUENCY TYPE D.C. TO 500 M.C. STANDARD CONTACT TYPE D.C. TO 30 M.C.

List Price

VERY HIGH FREQUENCY TYPE D C TO 300 M.C

PRICES-

FOB MOUNT VERNON, N. Y. TERMS—1% 10 DAYS, NET 30

THERMOCOUPLES ARE SUPPLIED
IN TWO SIZES:
1/2" DIAMETER x 1" LONG
7/16" DIAMETER x 3/4" LONG
CONNECTION LEADS 2 1/2" LONG

RESISTANCES ARE WITHIN ± 10% OF LISTED VALUES

LISTING OF STANDARD THERMOCOUPLES
INTERMEDIATE RANGES SUPPLIED TO ORDER
CORRESPONDENCE INVITED ON SPECIAL THERMOCOUPLES AND REQUIREMENTS

STANDARD CONTACT THERMOCOUPLES

						mint I lice	
Range		Code	Resis Heater	tance Couple	Couple Output Open Circuit	Quantity 1 - 4	Quantity 5 - 24*
1	MA	A	1800	12	6 Millivolts	\$27.00	\$18.00
1.5	MA	В	800	12	7 Millivolts	22.50	15.00
2	MA	С	750	12	7 Millivolts	18.00	12.00
5	MA	D	75	8	7 Millivolts	13.50	9.00
7.	MA	E	75	8	7 Millivolts	11.25	7.50
7.5	MA	F	40	8	7 Millivolts	11.25	7.50
10	MA	G	20	- 8	6 Millivolts	11.25	7.50
15	MA	H	14	4	7 Millivolts	11.25	7.50
20	MA	I	10	4	7 Millivolts	10.50	7.00
25	MA	J	7	4	7 Millivolts	10.50	7.00
50	MA	K	5	4	7 Millivolts	10.50	7.00
100	MA	L	2	4	7 Millivolts	10.50	7.00
150	MA	M	1.5	4	7 Millivolts	10.50	7.00
250	MA	N	.6	4	7 Millivolts	10.50	7.00
500	MA	0	.4	4	7 Millivolts	12.00	8.00
1000	MA	P	.25	4	7 Millivolts	12.00	8.00

FOR INSULATED HEATER THERMOCOUPLES — Add \$1.00 to Contact Price
*Quantity Discounts of 25 and Up Available Upon Request

A RECOMMENDED MILLIVOLTMETER FOR MEASURING
THERMOCOUPLE OUTPUTS IS
2 MILLIVOLTS, FULL SCALE
10 OHM RESISTANCE
200 MICROAMPERES FULL SCALE
(This allows the use of series
resistance which creates a
fast action instrument)

WHEN DESIGNING THERMO-COUPLE MEASURING CIRCUITS, DO NOT NEGLECT THE HEATER RESISTANCE OF THE THERMO-COUPLE USED

CASE MOUNTED THERMOCOUPLES AVAILABLE AT AN ADDITIONAL COST OF \$8.50 VACUUM THERMOCOUPLES are AC-DC transfer devices with true RMS response combined with high sensitivity and capable of high frequency operation. These extremely versatile devices are widely used for such purposes as:—

- Antenna current measurements
- Audio and RF generator output measurements
- High sensitivity (Up to 1000 ohms per volt) AC voltmeters
- True RMS current and voltage measurements for form factor determinations
- AC and DC voltmeters or ammeters in a single instrument
- AC measurements in cases of severe waveform variations such as random noise, speech or music voltages, spark discharges, etc.
- In analog type computations as squaring devices (The actual exponent varies from 1.88 to 1.99 under various conditions of operation)
- Numerous other applications where a DC output approximately proportional to the square of an input current, either AC or DC is required.