BUFFALO TUBE WORKSGENE	ERAL (%) ELECTRIC
R.O.P. W.E.M.	COMPANY
W.L.P. R.F.H.	
J.M.S. C.H.S. SCHI	ENECTADY, N. Y., U. S. A.
MAY 2 7 1946	
R.H.B. C.H.	
W.H.B. F.J.F. PATA	FOLDER No77879
W.C.L. IPBM PBM	
R.W.N. E.F.S.	IN PROMPTLY TO
Jan 1	Jefner FOR FILING
Title Certain Points	of View to be Considered in the Building
of a Pulse	Peak Emission and Characteristic Set
	Ву
Electr	ronic Tube Engineering Div.
Information prepared for	<u> </u>
D 41 - 1 - 1 - 1	
Tests made by	*
Information prepared by	P. W. Crapuchettes
Countersigned by	K. C. DeWalt
Date	Nov. 26, 1945

This folder is the property of the General Electric Company, and must not be retained except by special permission, or be used directly or indirectly in any way detrimental to the interest of the Company.

CERTAIN POINTS OF VITA TO B. CONSIDERED IN THE BUILDING OF A PULSE PEAK EMISSION & CHARACTERISTIC SET

The major components of the system will be separately discussed. Included are:

- A. Positive grid characteristic measurement
 - 1. Pulser
 - 2. Power Supply
 - 3. Energy Storage Capacitors
 - 4. Grid Voltage Measurement
 - 5. Grid Current Measurement
 - 6. Plate & Screen Current Measurement
- F. Emission Characteristics
 - 1. Fulser
 - 2. Peak Drive Measurement
 - 3. Current Viewing

Insofar as time permits, drawings will be prepared which illustrate the points mentioned,

- A. Positive Grid Characteristic Measurements
- A 4035 should be used. The ordinary 6SM7 synchronized driver can be used. The pulser plate supply should be capable of delivering 3.0 kV d=0 @ 100 ma approximately. With a 50 ohm pulse former (sinusoidal) this will develop about 8.0 kV maximum at the thyratron and approximately 7 kV peak at the load at a peak load current up to about 50 amperes. If it ever becomes necessary to deliver more current at this voltage, decrease the fixed loading.

A 1:1 inverting pulse transformer should be connected in series with the pulse forming circuit. The use of the transformer minimizes stray current effects, improving readings. The secondary should be loaded as shown on sketch #1 attached. The use of the split load resistor permits finer adjustment of drive at low levels (otherwise finest adjustment is limited by the volts per turn of the variac.

2. Plate and Screen Power Supplies

The supplies should be capable of delivering the
average current required without a noticeable reduction in volta
age from the no-load value. The average current is related to the
peak value by

(1) Ib or 102 = 2 Tpeak x pulse duration

If there is supply regulation, there will be an error in voltage reading. All supplies should be ungrounded.

The Energy Storage Capacitors
The plate voltage at the time of maximum plate current must be known. If the energy storage capacitor is large enough; the voltage will not drop off greatly during the pulse. Since Q E CV, it is easily shown that

(2) CLV = Ineak x pulse duration

Two alternative methods of measuring drive are feasibles synchroscopic measurement and peak voltmeter measurement. In D.F. # 77876 the synchroscopic measuring method is described. It is not a continuous reading instrument, therefore it is more difficult to adjust for particular conditions. This is particularly true when data for so measurement. (With the synchroscopic method it is necessary to guess at so measurement.)

A combination circuit is recommended, consisting of a synchroscope connection and a peak reading voltmeter. For low values of so the synchroscope should be used because it does not load the system. At low voltages, assuming scales are switched by changing the meter multiplier, the peak meter may load the system unnecessarily. In any event it would be well to observe grid drive pulse shape so that phase shifts can be noted (an indication of trouble). The recommended circuit is shown in sketch #2. An advantage of this system is that it reads so directly without separate measurement of bias.

5. Grid Current Messurement
D.F. \$77876 discusses the method recommended. Synchroscopic measurement should be used to separate positive and negative currents, enabling reading of data at the proper phase.

6. Flate and Screen Current Measurement
Multigrid tubes can produce very non-sinusoidal current
functions if a sinusoidal grid voltage pulse is applied. Therefore,
it is necessary to be certain that Eib and Eicz are read at the
proper phase. Whether or not amplifiers are used, it is well to
measure the currents synchroscopically.

When direct viswing the voltage developed across the viswing resistor may be an appreciable part of the supply voltage. Generally it cannot be neglected. If amplifiers were used, it would be possible to neglect this drop, resulting in direct reading of eb and so. It is recommended that a d-c amplifier be connected to the circuit, see sketch #3. The amplifier need not necessarily be linear, but the actual measurement is done on a comparative basis in the grid circuit of the amplifier.

A revision of the deflecting plates circuit should make is possible to introduce directly viewed signals to one electrode and amplified signals to the other. The amplifier should be made in accordance with accepted video practice. It should be physically located alongside the deflector terminal, reducing reactive loading of the amplifier. No cables or shielding should be used in the output circuit. The grid circuit of the amplifier should be cable connected to the viewing resistor in the conventional way. The amplifier should receive essentially positive pulses and be biased off so that no saturation ever occurs, comparison being in the grid circuit. Comparative circuits for direct and amplified viewing should be independent and switched along with signal circuits (see sketch #1).

The use of current viewing amplifiers is to be recommended whenever so 2000 v or less. Above 2000 v the error introduced by neglecting the viewed voltage is small. However, special care must be exercised in designing viewing resistors to avoid self-inductance in the resistor. In very high current cases direct viewing, with correction for resistor drop, is more accurate.

B. Imission Characteristics

1. Pulser

The 4035 pulser described above should be used to drive a 1821 pulser when peak drive above 50 amperes is required. The 1821 should be supplied with 4000 Vdc. It has been used at currents up to 400 amperes, and it is possible to run above this value if the tube is adequately cooled. The 1821 current will probably be about twice the useful load current. Use a 131 inverting transformer.

2. Peak Drive Measurement
The combination of peak voltmeter and synchroscope should be used.

3. Current Viewing
Direct synchroscopic measurement is recommended here.
The situation is much like that in the grid circuit of the characteristic set. More accuracy can be obtained.

Procedure for the use of Direct Viewing and Amplifying Circuit

The circuit shown on sketch #3 provides direct viewing and amplified viewing. Two vertical centering controls are supplied, assuming that it will be expedient to switch centering controls along with the signal circuits. The two calibrating controls are not switched though it would be desirable to short out the bias (emplifier calibrator) when direct reading and to switch the present celibrator to "off" when reading with the amplifier.

The synchroscope is centered for each use by the separate centering controls, both calibrating voltages being zero at the time of centering. When a pulse is applied to the amplifier, its magnitude is determined by increasing the bias until the peak of the trace has returned to the centered position. When direct reading use present practice.


P. W. Crapuchettes Nov 26, 1945.

ENGINEERING TUBE DIVISION

Countersigned: KCDeWalt
Nov 26, 1945


11-23-45

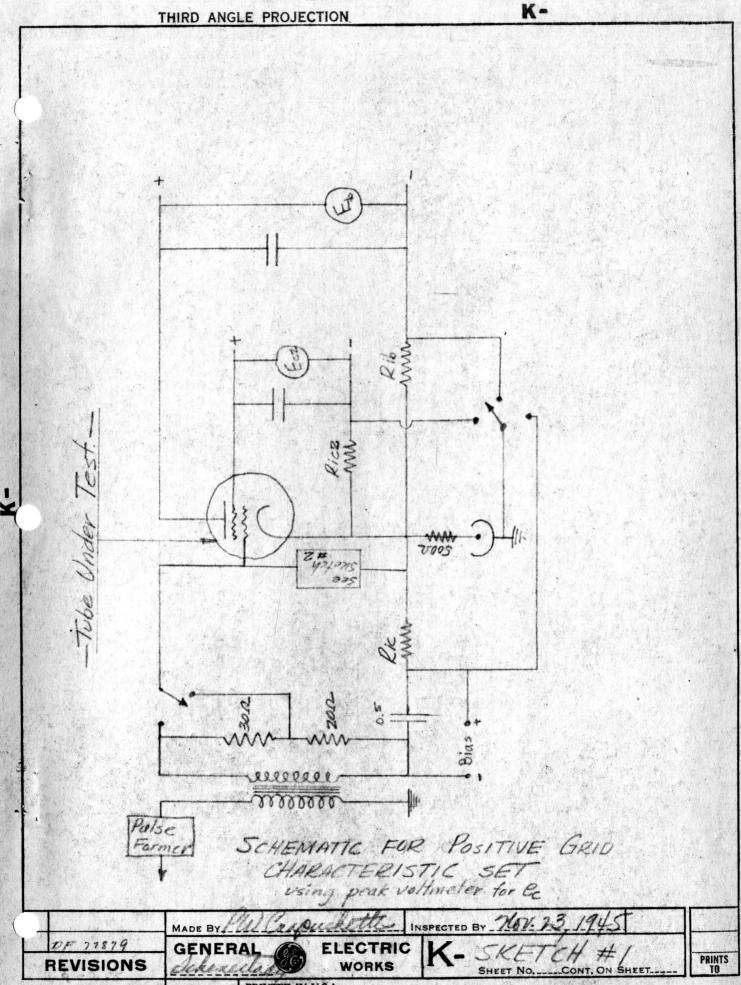TA Elder KC D Walt EF Peterson CR Knight BS Angwin PW Crapuchettes (OW Pike (AC Gable



FF-449-A (1-41)

PRINTED IN U.S.A.

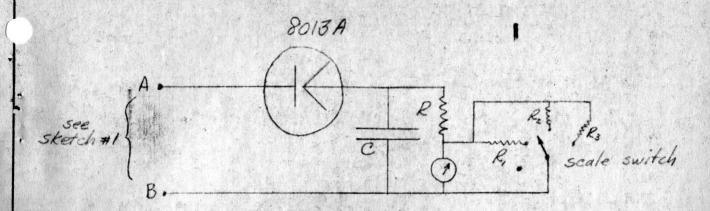

Note 1: This circuit reads actual peak grid volts, including bias.

NOTE 2: RC product should be nearly unity.

Note 3: R., Rz, and Rz should be adjusted to read 1500, 500 v, 15000 and 50000 full scale.

Note 4: K-69087-1A117 gives the capacity dividing circuit. See D.F. 17876.

Note 5: 8016 or 8013A are good diodes to use. 8013A is better because of less impedance.

DF 27879

FF-449-A (1-41)

GENERAL

ELECTRIC WORKS K- SKETCH # Z SHEET NO. CONT. ON SHEET

PRINTS 10

